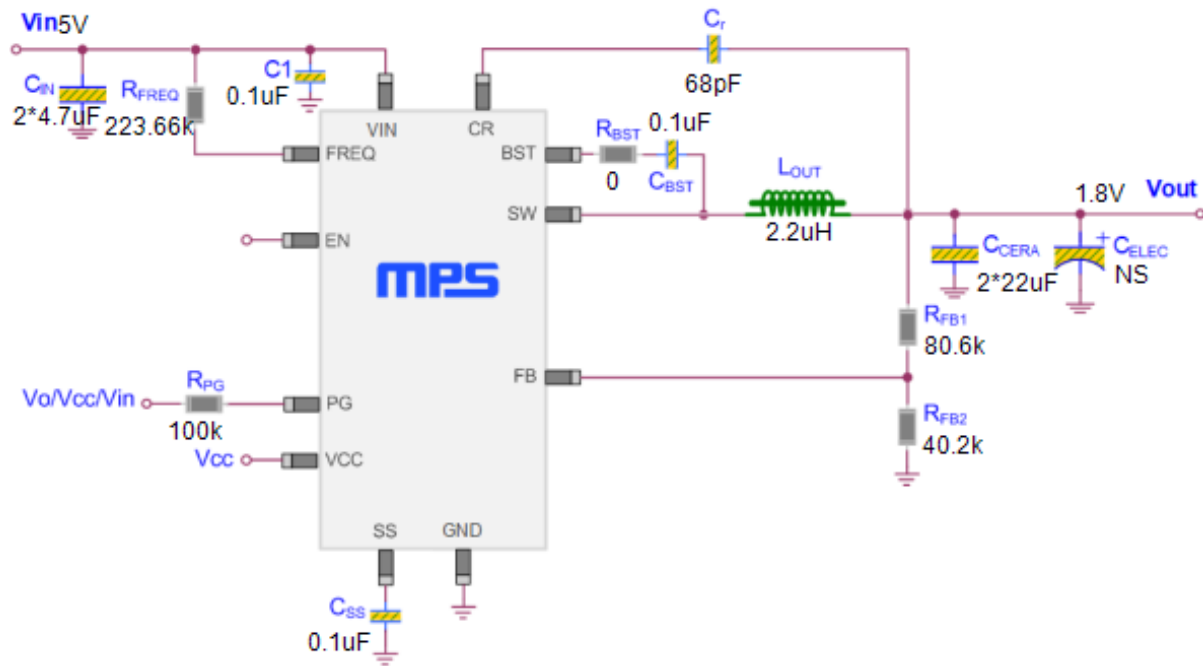



Schematic





Spec Analysis

Parameter	Result	Minimum	Maximum
Constant-On-Time Control(Y/N)	Y		
Input Voltage(V)	5		
Min. Input Voltage(V)	5		
Max. Input Voltage(V)	7		
Output Voltage(V)	1.8		
Output Current(A)	3		
Frequency(kHz)	500		
Slope Ripple (mV)	38		
Input Voltage Ripple(mV)	162.1		
Output Voltage Ripple(mV)	7.3		
Inductor Peak-Peak Current(A)	1.05	2.48	3.52
Efficiency(%)	86.64		

Waveforms

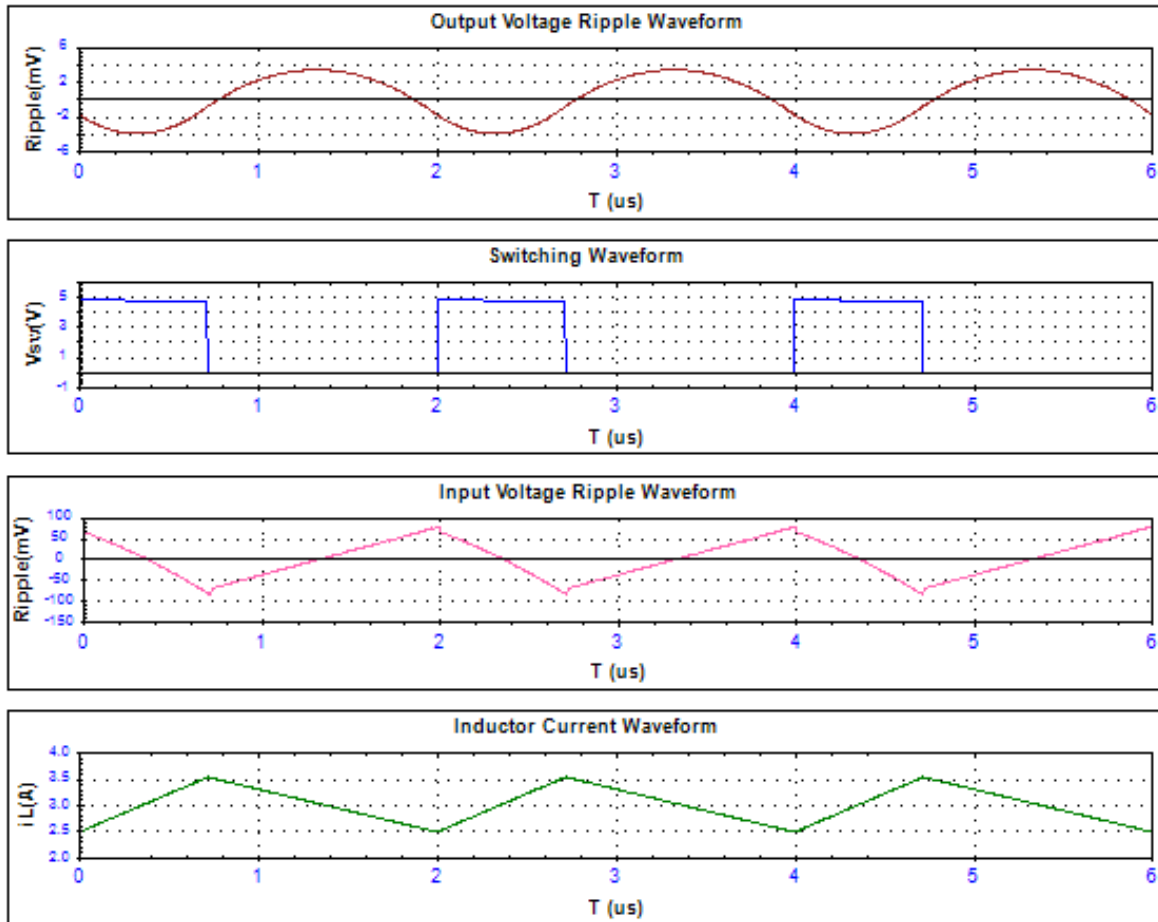

Efficiency & Power Loss Analysis

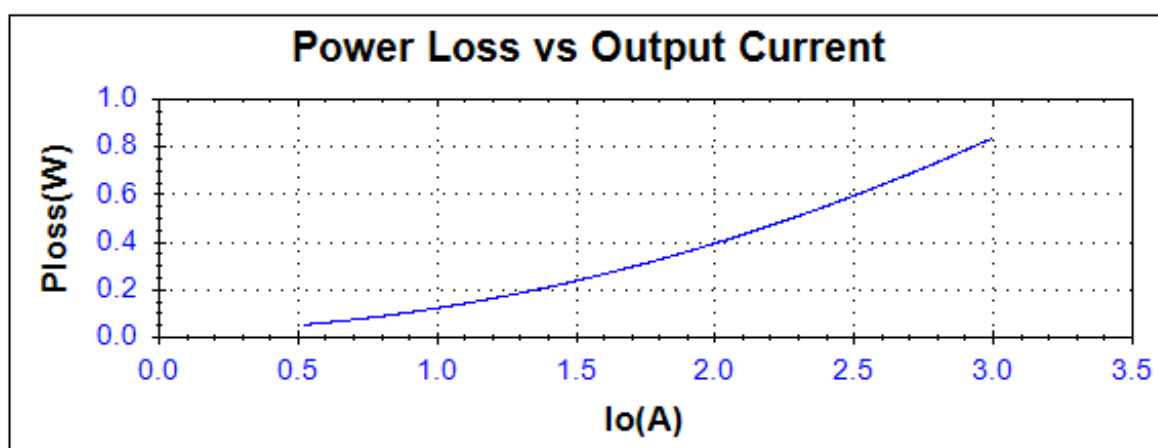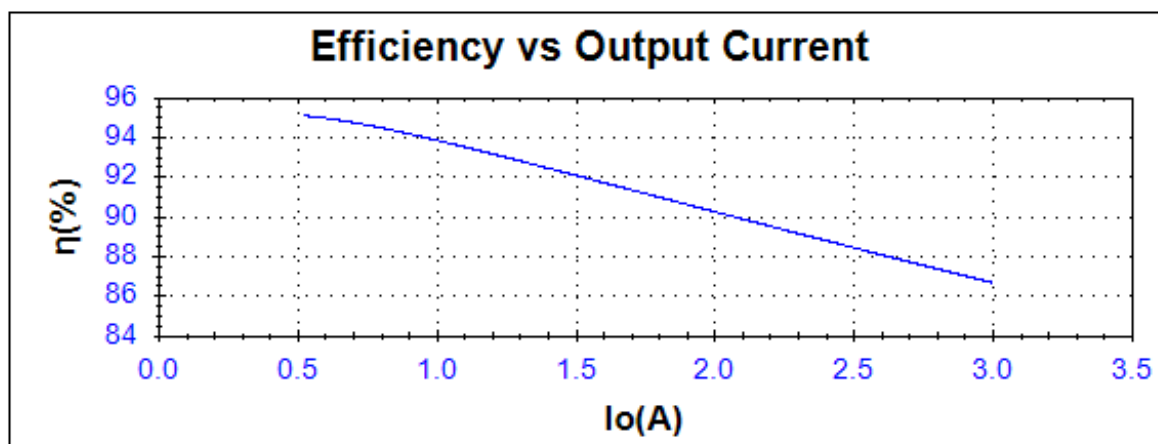

Bill of Materials

Quantity	Parameter	Value	Description	Package	Vendor	Part Number
2	Cin	4.7uF	10V, X5R, Ceramic	0402	Würth Elektronik	885012105026
1	C1	0.1uF	50V, Ceramic	0603	Any	
2	Ccera	22uF	6.3V, X5S, Ceramic	0805	muRata	GRM21BC60J2 26M
	Celec		NS			
1	Cr	68pF	50V, , Ceramic	0603	Any	
1	CSS	0.1uF	50V, Ceramic	0603	Any	
1	CBST	0.1uF	50V, Ceramic	0603	Any	
1	RPG	100k	5%	0603	Any	
1	RBST	0	5%	0603	Any	
1	RFB1	80.6k	1%	0603	Any	
1	RFB2	40.2k	1%	0603	Any	
1	RFREQ	223.66k	1%	0603	Any	
1	LOUT	2.2uH	32mOhm,6.7A	SMT	Würth Elektronik	744373344802 2
1	U1	-	Cot, 500kHz, 19V, 4A	QFN2x3-14	MPS	MP2326

Note:

- 1) More details information please reference the device datasheets and/or application notes.
- 2) Please note too large output capacitance may lead to startup problems.

Layout Info

PCB layout is very important to achieve stable operation. Please follow these guidelines and take the figures for reference. The layout figure is from datasheet, please refer to datasheet's typical application circuit as corresponding schematic.

- 1) Keep the power loop of input capacitor, HS switch, LS switch as small as possible.
- 2) Keep the connection of input capacitor and IN pin as short and wide as possible.
- 3) Ensure all feedback connections are short and direct. Place the feedback resistors and compensation components as close to the chip as possible.
- 4) Route SW away from sensitive analog areas such as FB.
- 5) Connect IN, SW, and especially GND respectively to a large copper area to cool the chip to improve thermal performance and long-term reliability.
- 6) Adding RC snubber circuit from IN pin to SW pin can reduce SW spikes.

